

XOR Revisited

XOR is also called modulo-2 addition.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


$A \oplus B = 1$ only when there are an odd number of 1's in (A,B). The same is true for $A \oplus B \oplus C$ also.

$$\left. \begin{array}{l} 1 \oplus A = \overline{A} \\ 0 \oplus A = A \end{array} \right\}$$

Why?

Logic Design Examples


Half Adder

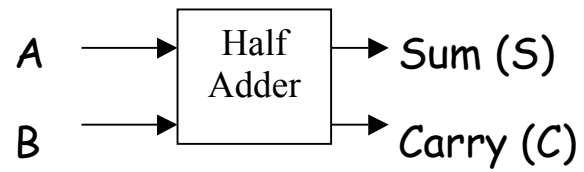


A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \oplus B$$

$$C = A.B$$

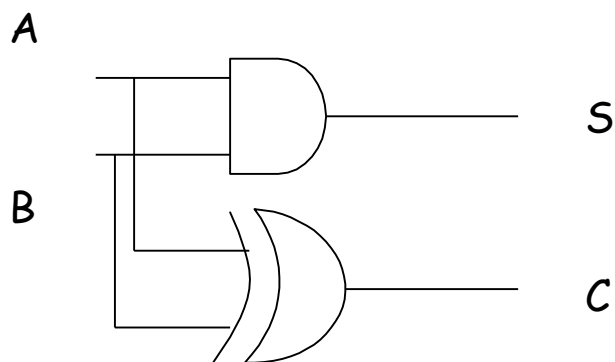

Full Adder

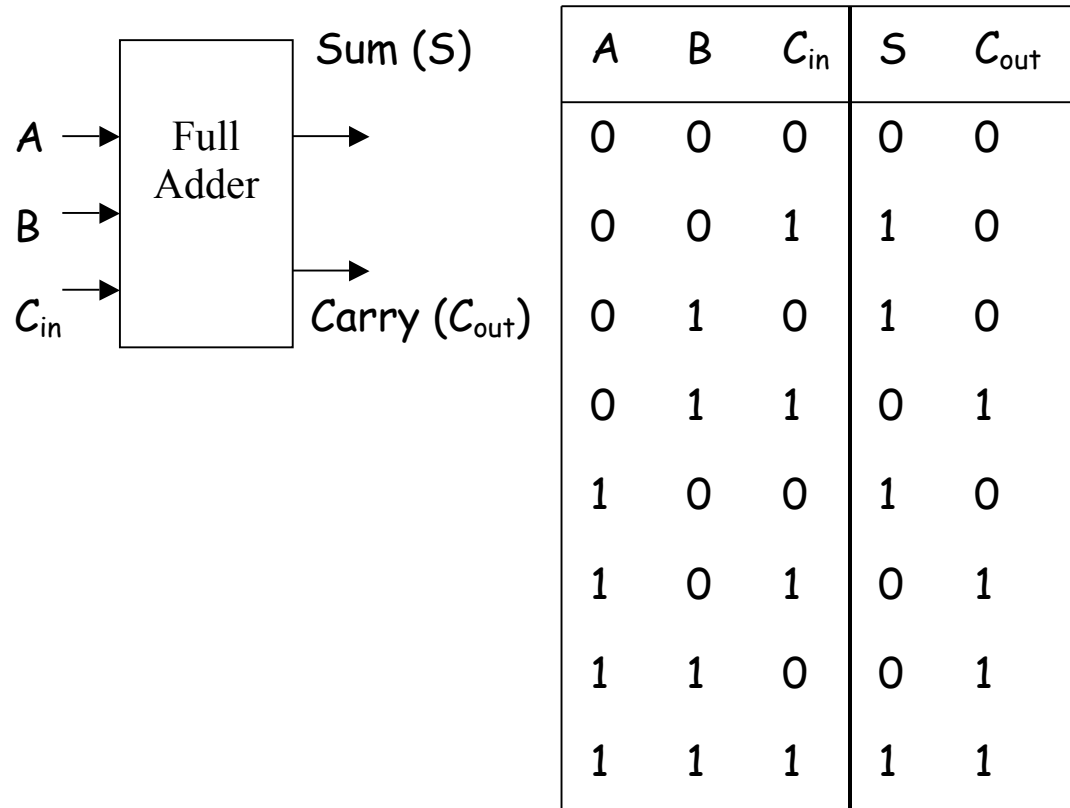


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = A.B + B.C_{in} + A.C_{in}$$

Can you design a full adder using two half-adders
(and a few gates if necessary)?

Decoders

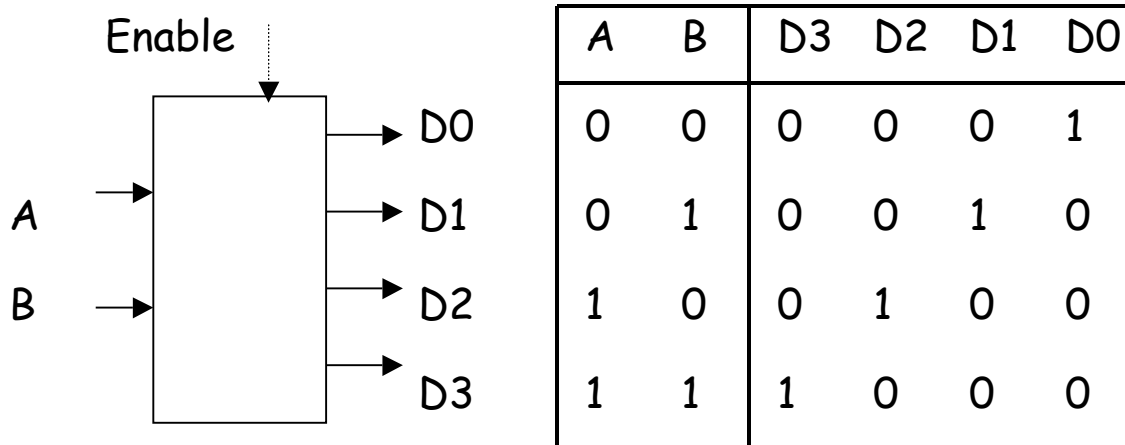A typical decoder has n inputs and 2^n outputs.



A 2-to-4 decoder and its truth table

$$D3 = A.B$$

$$D2 = A.\bar{B}$$

$$D1 = \bar{A}.B$$

$$D0 = \bar{A}.\bar{B}$$

Draw the circuit of this decoder.


The decoder works per specs when (**Enable = 1**). When **Enable = 0**, all the outputs are 0.

Exercise. Design a 3-to-8 decoder.

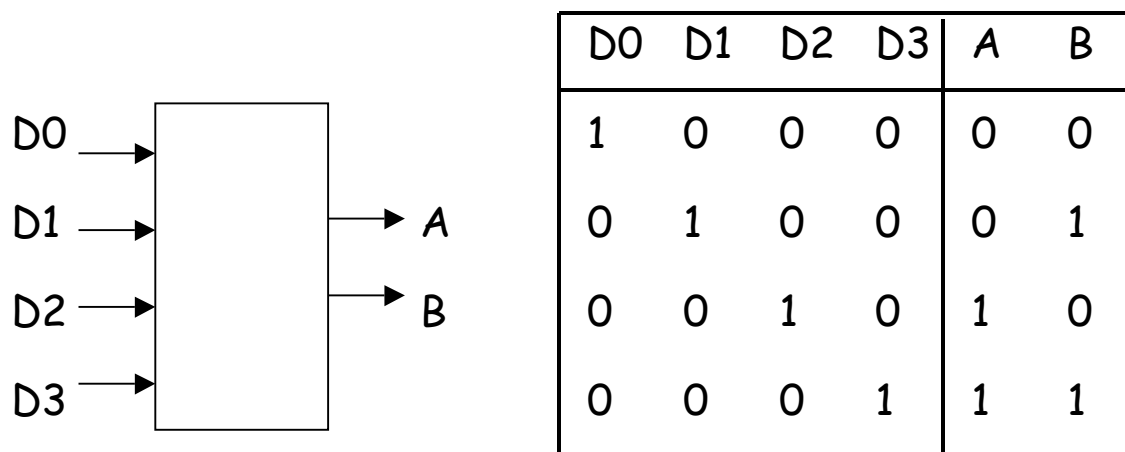Question. Where are decoders used?

Encoders

A typical encoder has 2^n inputs and n outputs.




A 4-to-2 encoder and its truth table

$$A = D1 + D3$$
$$B = D2 + D3$$

Multiplexor

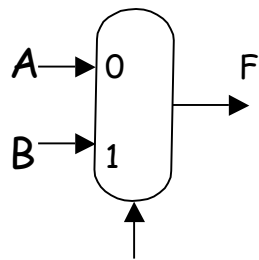It is a **many-to-one switch**, also called a **selector**.



Control S

$$S = 0, F = A$$

$$S = 1, F = B$$

Specifications of the mux

A 2-to-1 mux

$$F = \overline{S} \cdot A + S \cdot B$$

Exercise. Design a 4-to-1 mux.