

# Floating point operations in MIPS

**32 separate single precision** FP registers in MIPS

f0, f1, f2, ... f31,

Can also be used as **16 double precision** registers

f0, f2, f4, f30 (f0 means f0,f1 f2 means f2,f3)

These reside in a **coprocessor C1** in the same package

## Operations supported

add.**s**      \$f2, \$f4, \$f6      # f2 = f4 + f6 (single precision)

add.**d**      \$f2, \$f4, \$f6      # f2 = f4 + f6 (double precision)

(Also subtract, multiply, divide format are similar)

lwc1      \$f1, 100(\$s2)      # f1 = M [s2 + 100]      (32-bit load)

mtc1      \$t0, \$f0      # f0 = t0 (move to coprocessor 1)

mfc1      \$t1, \$f1      # t1 = f1 (move from coprocessor 1)

## Sample program

### Evaluation of a Polynomial $a.x^2 + b.x + c$

```
# $f0 --- x
# $f2 --- sum of terms
.....
# Evaluate the quadratic
l.s      $f2,a      # sum = a
mul.s    $f2,$f2,$f0 # sum = ax

l.s      $f4,b      # get b
add.s    $f2,$f2,$f4 # sum = ax + b
mul.s    $f2,$f2,$f0 # sum = (ax+b)x = ax^2 + bx


l.s      $f4,c      # get c
add.s    $f2,$f2,$f4 # sum = ax^2 + bx + c
.....

.data
a: .float 1.0
b: .float 1.0
c: .float 1.0
```

Pseudo-  
instruction
 
# Sequential Circuits


The output depends not only on the current inputs, but also on the past values of the inputs.



An SR Latch


S	R	Q	$\bar{Q}$	Comment
0	0	0/1	1/0	Old state continues
1	0	1	0	Set state
0	1	0	1	Reset state
1	1	0	0	Illegal inputs

## A clocked D-latch

 


Clock is the enabler. If  $C=0$ ,  $Q$  remains unchanged.

 When  $C=1$ , then  $Q$  acquires the value of  $D$ . We will use it as a building block of sequential circuits.




There are some shortcomings of this simple circuit. An **edge-triggered** circuit (or a **master-slave** circuit) solves this problem (to be discussed in the class)

## Master-Slave D flip-flop

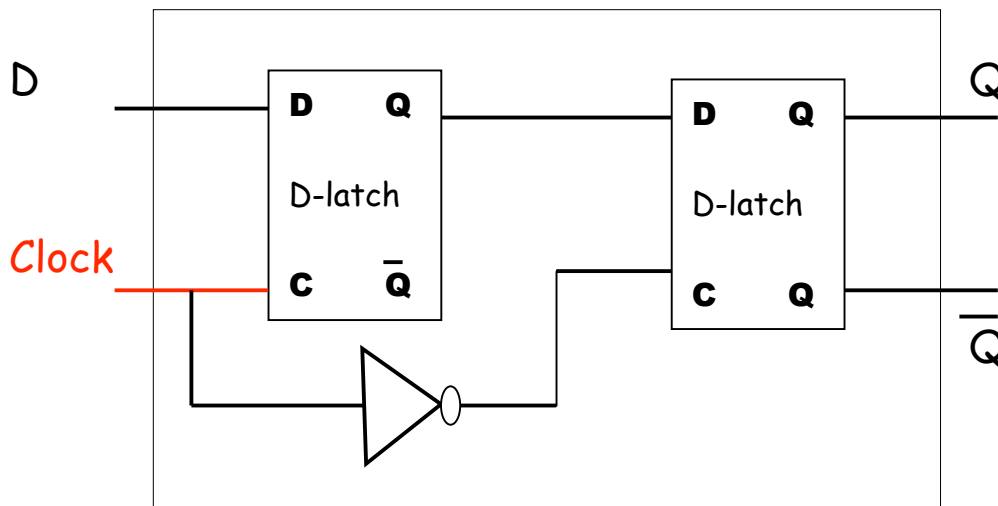

Internal details shown

 



Clock pulse

Abstract view

The output Q acquires the value of the input D, only when **one complete clock pulse** is applied to the clock input.
 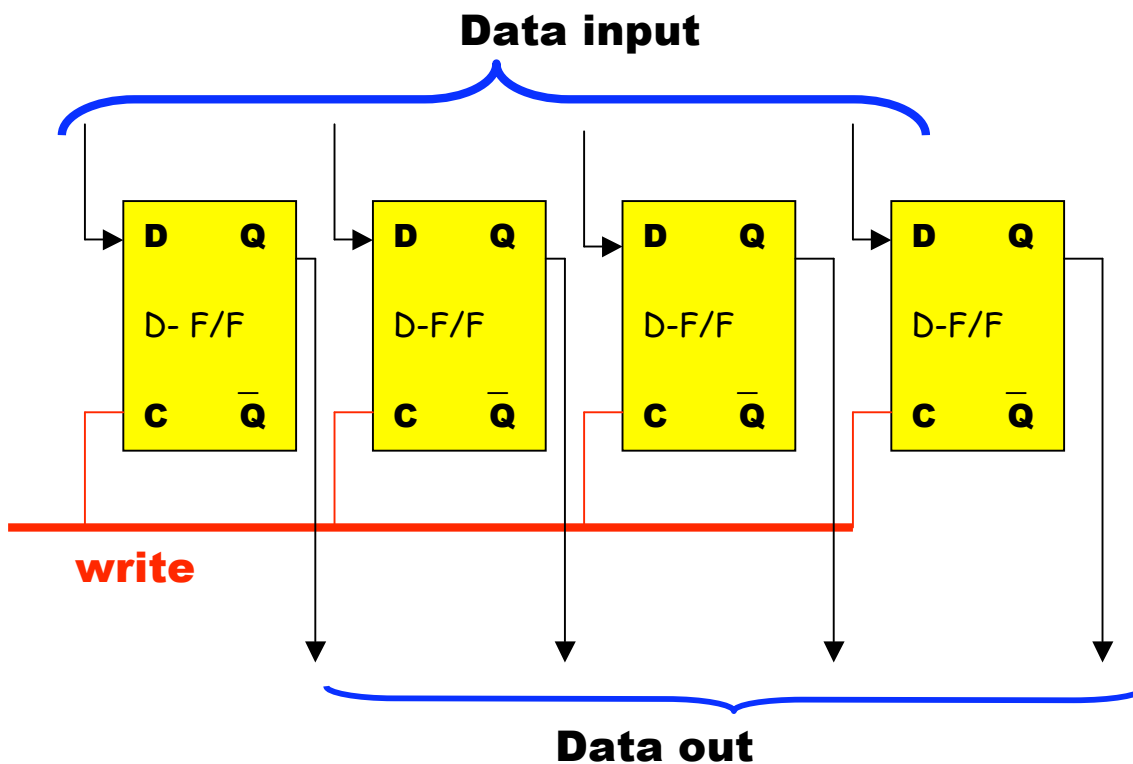
## Register

A 8-bit register is an array of 8 D-flip-flops.







Abstract view of a register

### Binary counter

Counts 0, 1, 2, 3, ...

 

 A toggle flip-flop (T) is a **modulo-2 counter**




**A 4-bit counter**  
(mod-16counter)

Observe how Q3 Q2 Q1 Q0 change when pulses are applied to the clock input


## State diagram of a 4-bit counter

Here state = Q3Q2Q1Q0

 

Recall that the program counter is a 32-bit counter

## A shift register

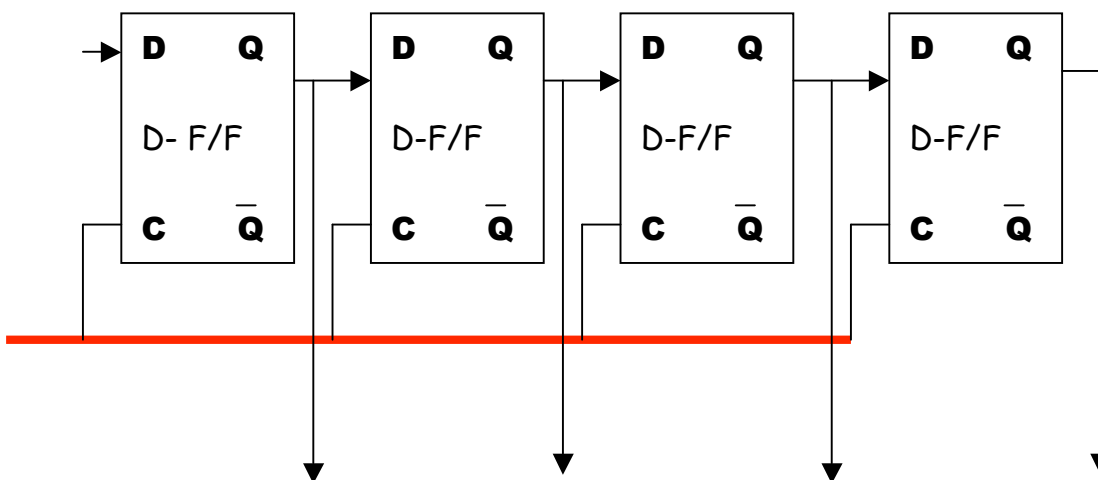



## Shift (right)

With each pulse on the shift input, data moves by pulse to the right.